

Hundred capacitors connected in series/parallel. We have a set of 100 capacitors of arbitrary geometries, with different capacitances C_1, C_2, \dots, C_{100} . Let C_{series} and C_{parallel} be the equivalent total capacitances of the capacitors connected in series [Fig. Q2.11(a)] and parallel [Fig. Q2.11(b)], respectively. Comparing these two equivalent capacitances, we have

- (A) $C_{\text{series}} < C_{\text{parallel}}$.
- (B) $C_{\text{series}} = C_{\text{parallel}}$.
- (C) $C_{\text{series}} > C_{\text{parallel}}$.
- (D) Depends on the geometries of the individual capacitors and nothing else.
- (E) Depends on the relationship between particular values of C_1, C_2, \dots, C_{100} .

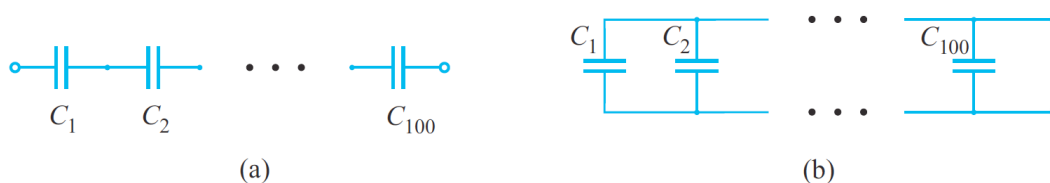


Figure Q2.11 Set of 100 arbitrary capacitors connected in series (a) and parallel (b); for Question 2.25.

Solution: (A)

Answer: (A)